



## SYNCHRONOUS COUNTER DESIGN

A synchronous counter is kind of counter (in contrast to an asynchronous counter) whose output bits change state simultaneously, with no ripple. The only way we can build such a counter circuit is to connect all the clock inputs together, so that each and every flip-flop receives the exact same clock pulse at the exact same time. Procedure to design synchronous counter are as follows.

Designing synchronous mod 5 counter using D Flip Flops, counting up.

1. Create state transition table for counter:

$S_n$ (Present state)				$S_{n+1}$ (Next state)			
Q <sub>DEC</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>DEC</sub>
0	0	0	0	0	0	1	1
1	0	0	1	0	1	0	2
2	0	1	0	0	1	1	3
3	0	1	1	1	0	0	4
4	1	0	0	0	0	0	0

2. Determine number of Flip-Flops used.

3. Using state transition table for counter and Flip-Flop excitation table create and simplify the function of each Flip-Flop input using Karnaugh map.

*D Flip-Flop excitation table:*

Q <sub>n</sub>	Q <sub>n+1</sub>	D
0	0	0
0	1	1
1	0	0
1	1	1

*Karnaugh map for D<sub>0</sub>:*

Q <sub>2</sub> \ Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
0	1	0	0	1
1	0	-	-	-

$$D_0 = \overline{Q_0} \overline{Q_2} = \overline{Q_0 + Q_2}$$



Karnaugh map for D1:

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	1	0	1
1	0	-	-	-


$$D_1 = Q_0 \overline{Q_1} + \overline{Q_0} Q_1$$

Karnaugh map for D2:

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	0	1	0
1	0	-	-	-

$$D_2 = Q_0 Q_1$$

4. Draw the circuit.

 

Rys 1: Mod 5 counter

T Flip-Flop excitation table:

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

JK Flip-Flop excitation table:

$Q_n$	$Q_{n+1}$	J	K
0	0	0	-
0	1	1	-
1	0	-	1
1	1	-	0